
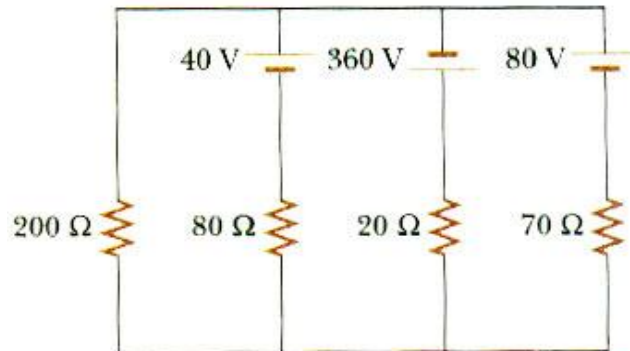


Homework #8

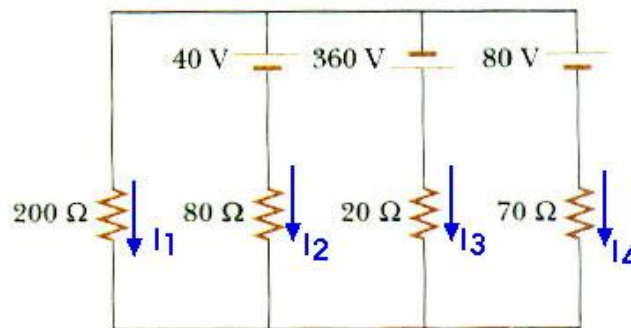In the circuit of Figure below, determine the current in each resistor and the voltage across the 200-ohm resistor.



This requires the application of **Kirchoff's Rules**. Begin by assigning a current through each of the resistors.




Apply Kirchoff's **Junction Rule** at the two junctions.


J1: $I_1 + I_2 = I_5$

J2: $I_5 + I_3 + I_4 = 0$

$I_1 + I_2 + I_3 + I_4 = 0$

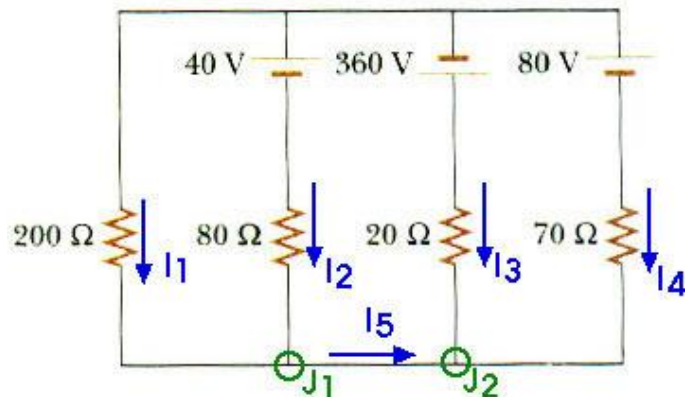

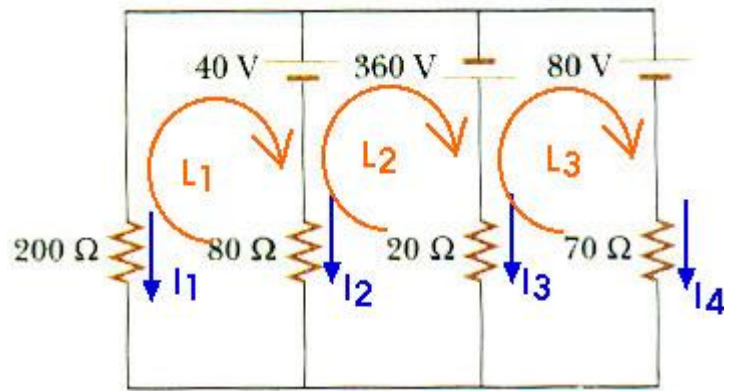Certainly one or more of our currents will turn out to be **negative**. (That's **okay!**) We have **four** unknowns and only one equation. We will have to get **three** more equations from Kirchoff's **Loop Rule**.



L1: $-40 \text{ V} = I_2 (80 \Omega) - I_1 (200 \Omega)$

L2: $40 \text{ V} - 360 \text{ V} = I_3 (20 \Omega) - I_2 (80 \Omega)$

L3: $-360 \text{ V} - 80 \text{ V} = I_4 (70 \Omega) - I_3 (20 \Omega)$

We are finished with the "Physics" of this problem. It's "just" math from here on. We have **four unknowns** so now we need only **four equations**,

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$-40 \text{ V} = I_2 (80 \Omega) - I_1 (200 \Omega)$$

$$40 \text{ V} - 360 \text{ V} = I_3 (20 \Omega) - I_2 (80 \Omega)$$

$$-360 \text{ V} - 80 \text{ V} = I_4 (70 \Omega) - I_3 (20 \Omega)$$

$$80 \text{ V} = I_4 (70 \Omega) - I_1 (200 \Omega)$$

$$\begin{aligned} I_1 + I_2 + I_3 + I_4 &= 0 \\ -200I_1 + 80I_2 &= -40 \text{ A} \\ -80I_2 + 20I_3 &= -320 \text{ A} \\ -20I_3 + 70I_4 &= -440 \text{ A} \end{aligned}$$

$$\begin{aligned} I_1 + I_2 + I_3 + I_4 &= 0 \\ -20I_1 + 8I_2 &= -4 \\ -8I_2 + 2I_3 &= -32 \\ -2I_3 + 7I_4 &= -44 \end{aligned}$$

$$\begin{array}{rcl}
 20I_1 + 20I_2 + 20I_3 + 20I_4 & = & 0 \\
 -20I_1 + 8I_2 & = & -4 \\
 \hline
 28I_2 + 20I_3 + 20I_4 & = & -4
 \end{array}$$

$$\begin{array}{rcl}
 14I_2 + 10I_3 + 10I_4 & = & -2 \\
 -8I_2 + 2I_3 & = & -32 \\
 -2I_3 + 7I_4 & = & -44
 \end{array}$$

$$\begin{array}{rcl}
 112I_2 + 80I_3 + 80I_4 & = & -16 \\
 -112I_2 + 28I_3 & = & -448 \\
 \hline
 108I_3 + 80I_4 & = & -464 \\
 27I_3 + 20I_4 & = & -116
 \end{array}$$

$$\begin{array}{rcl}
 27I_3 + 20I_4 & = & -116 \\
 -2I_3 + 7I_4 & = & -44
 \end{array}$$

$$\begin{array}{rcl}
 54I_3 + 40I_4 & = & -232 \\
 -54I_3 + 189I_4 & = & -1188 \\
 \hline
 229I_4 & = & -1420
 \end{array}$$

$$I_4 = -\frac{1420}{229}$$

$$I_4 = -6.2014$$

$$\begin{array}{rcl}
 -2I_3 + 7I_4 & = & -44 \\
 -2I_3 + 7(-6.201) & = & -44 \\
 -2I_3 - 43.406 & = & -44 \\
 -2I_3 & = & -44 + 43.406 \\
 -2I_3 & = & -0.594 \\
 I_3 & = & \frac{0.594}{2} \\
 I_3 & = & +0.297
 \end{array}$$

$$-8I_2 + 2I_3 = -4$$

$$-8I_2 + 2(+0.297) = -4$$

$$-8I_2 + 0.594 = -4$$

$$-8I_2 = -4 - 0.594$$

$$-8I_2 = -4.594$$

$$I_2 = \frac{4.594}{8}$$

$$I_2 = 0.574 \text{ A}$$

$$-200I_1 + 80I_2 = -40$$

$$-200I_1 + 80(0.574) = -40$$

$$-200I_1 + 45.939 = -40$$

$$-200I_1 = -40 - 45.939$$

$$-200I_1 = -85.939$$

$$I_1 = \frac{85.939}{200}$$

$$I_1 = 0.430 \text{ A}$$

$$I_2 = 0.574 \text{ A}$$

$$I_3 = 0.297 \text{ A}$$

$$I_4 = -6.201 \text{ A}$$

Deciding how to choose a "loop" sometimes seems difficult. **Any** continuous loop is a candidate. We might have used a loop around the **outside** of the entire circuit diagram.

